**Problem 2.9** A transmission line operating at 125 MHz has  $Z_0 = 40 \Omega$ ,  $\alpha = 0.02$  (Np/m), and  $\beta = 0.75$  rad/m. Find the line parameters R', L', G', and C'.

**Solution:** Given an arbitrary transmission line, f = 125 MHz,  $Z_0 = 40 \Omega$ ,  $\alpha = 0.02$  Np/m, and  $\beta = 0.75$  rad/m. Since  $Z_0$  is real and  $\alpha \neq 0$ , the line is distortionless. From Problem 2.6,  $\beta = \omega \sqrt{L'C'}$  and  $Z_0 = \sqrt{L'/C'}$ , therefore,

$$L' = \frac{\beta Z_0}{\omega} = \frac{0.75 \times 40}{2\pi \times 125 \times 10^6} = 38.2 \text{ nH/m}.$$

Then, from  $Z_0 = \sqrt{L'/C'}$ ,

$$C' = \frac{L'}{Z_0^2} = \frac{38.2 \text{ nH/m}}{40^2} = 23.9 \text{ pF/m}.$$

From  $\alpha = \sqrt{R'G'}$  and R'C' = L'G',

$$R' = \sqrt{R'G'}\sqrt{\frac{R'}{G'}} = \sqrt{R'G'}\sqrt{\frac{L'}{C'}} = \alpha Z_0 = 0.02 \text{ Np/m} \times 40 \Omega = 0.8 \Omega/\text{m}$$

and

$$G' = \frac{\alpha^2}{R'} = \frac{(0.02 \text{ Np/m})^2}{0.8 \Omega/\text{m}} = 0.5 \text{ mS/m}.$$