

**Problem 2.29** A 50-MHz generator with  $Z_g = 50 \Omega$  is connected to a load  $Z_L = (50 - j25) \Omega$ . The time-average power transferred from the generator into the load is maximum when  $Z_g = Z_L^*$ , where  $Z_L^*$  is the complex conjugate of  $Z_L$ . To achieve this condition without changing  $Z_g$ , the effective load impedance can be modified by adding an open-circuited line in series with  $Z_L$ , as shown in Fig. 2-40 (P2.29). If the line's  $Z_0 = 100 \Omega$ , determine the shortest length of line (in wavelengths) necessary for satisfying the maximum-power-transfer condition.

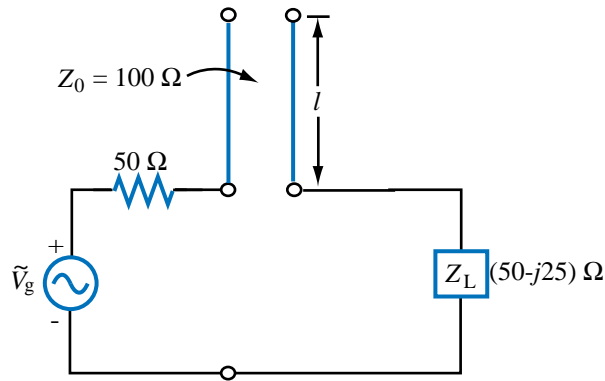


Figure P2.29: Transmission-line arrangement for Problem 2.29.

**Solution:** Since the real part of  $Z_L$  is equal to  $Z_g$ , our task is to find  $l$  such that the input impedance of the line is  $Z_{in} = +j25 \Omega$ , thereby cancelling the imaginary part of  $Z_L$  (once  $Z_L$  and the input impedance the line are added in series). Hence, using Eq. (2.73),

$$-j100 \cot \beta l = j25,$$

or

$$\cot \beta l = -\frac{25}{100} = -0.25,$$

which leads to

$$\beta l = -1.326 \text{ or } 1.816.$$

Since  $l$  cannot be negative, the first solution is discarded. The second solution leads to

$$l = \frac{1.816}{\beta} = \frac{1.816}{(2\pi/\lambda)} = 0.29\lambda.$$