

**Problem 2.50** Generate a bounce diagram for the voltage  $V(z, t)$  for a 1-m long lossless line characterized by  $Z_0 = 50 \Omega$  and  $u_p = 2c/3$  (where  $c$  is the velocity of light) if the line is fed by a step voltage applied at  $t = 0$  by a generator circuit with  $V_g = 60 \text{ V}$  and  $R_g = 100 \Omega$ . The line is terminated in a load  $Z_L = 25 \Omega$ . Use the bounce diagram to plot  $V(t)$  at a point midway along the length of the line from  $t = 0$  to  $t = 25 \text{ ns}$ .

**Solution:**

$$\Gamma_g = \frac{R_g - Z_0}{R_g + Z_0} = \frac{100 - 50}{100 + 50} = \frac{50}{150} = \frac{1}{3},$$

$$\Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{25 - 50}{25 + 50} = \frac{-25}{75} = -\frac{1}{3}.$$

From Eq. (2.124b),

$$V_1^+ = \frac{V_g Z_0}{R_g + Z_0} = \frac{60 \times 50}{100 + 50} = 20 \text{ V}.$$

Also,

$$T = \frac{l}{u_p} = \frac{l}{2c/3} = \frac{3}{2 \times 3 \times 10^8} = 5 \text{ ns}.$$

The bounce diagram is shown in Fig. P2.50(a) and the plot of  $V(t)$  in Fig. P2.50(b).

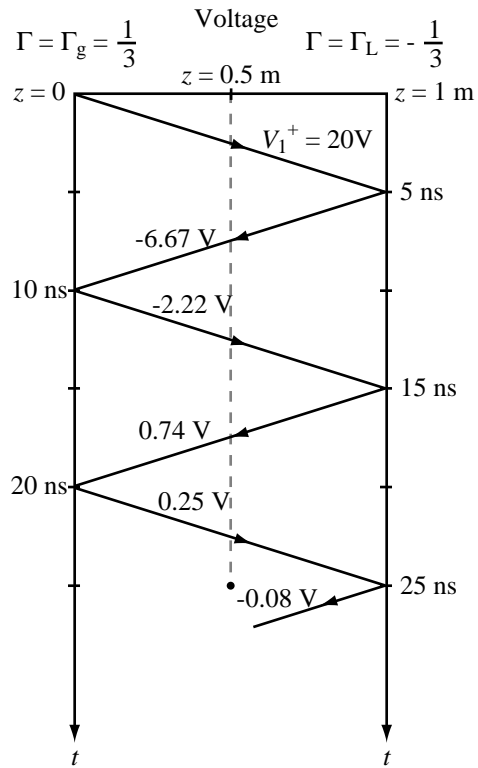


Figure P2.50: (a) Bounce diagram for Problem 2.50.

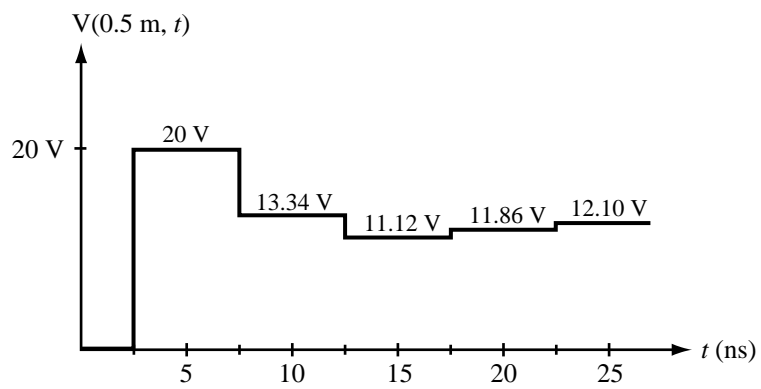


Figure P2.50: (b) Time response of voltage.