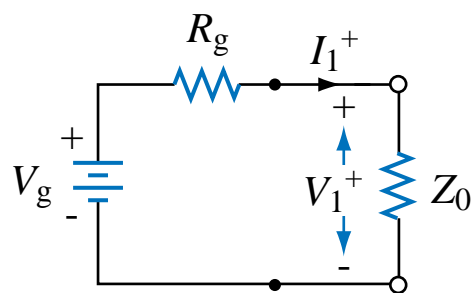


(a) Transmission-line circuit



(b) Equivalent circuit at  $t=0^+$

Figure 2-33